

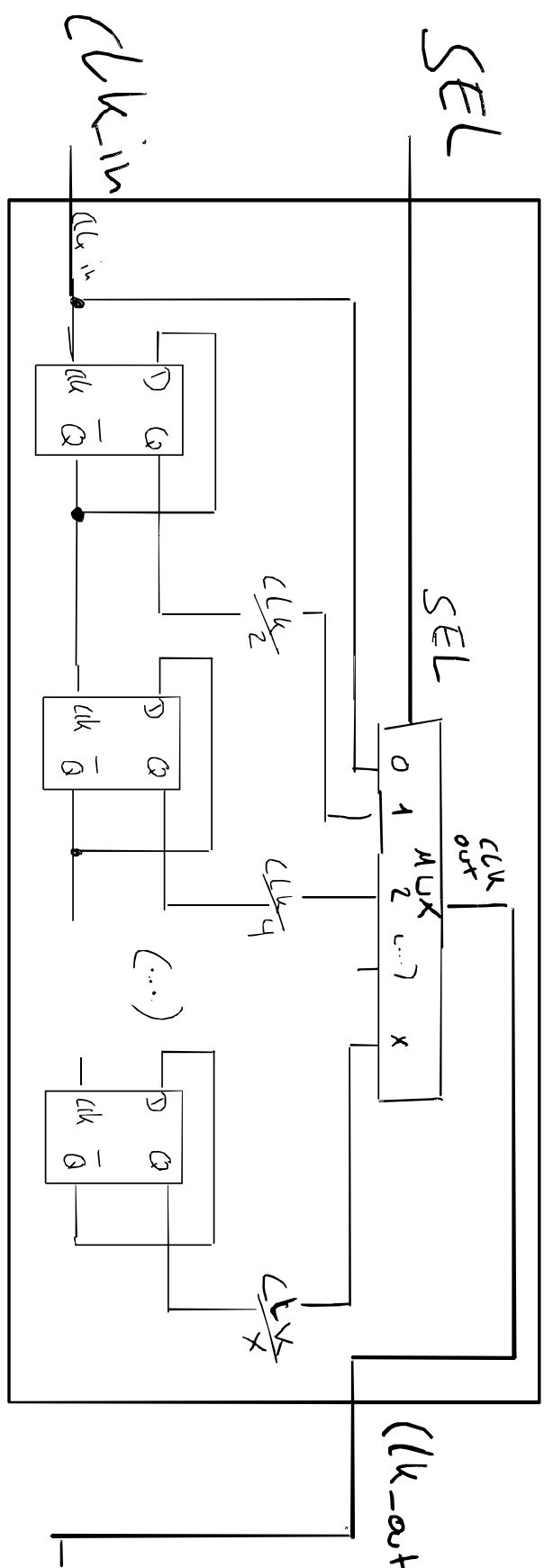


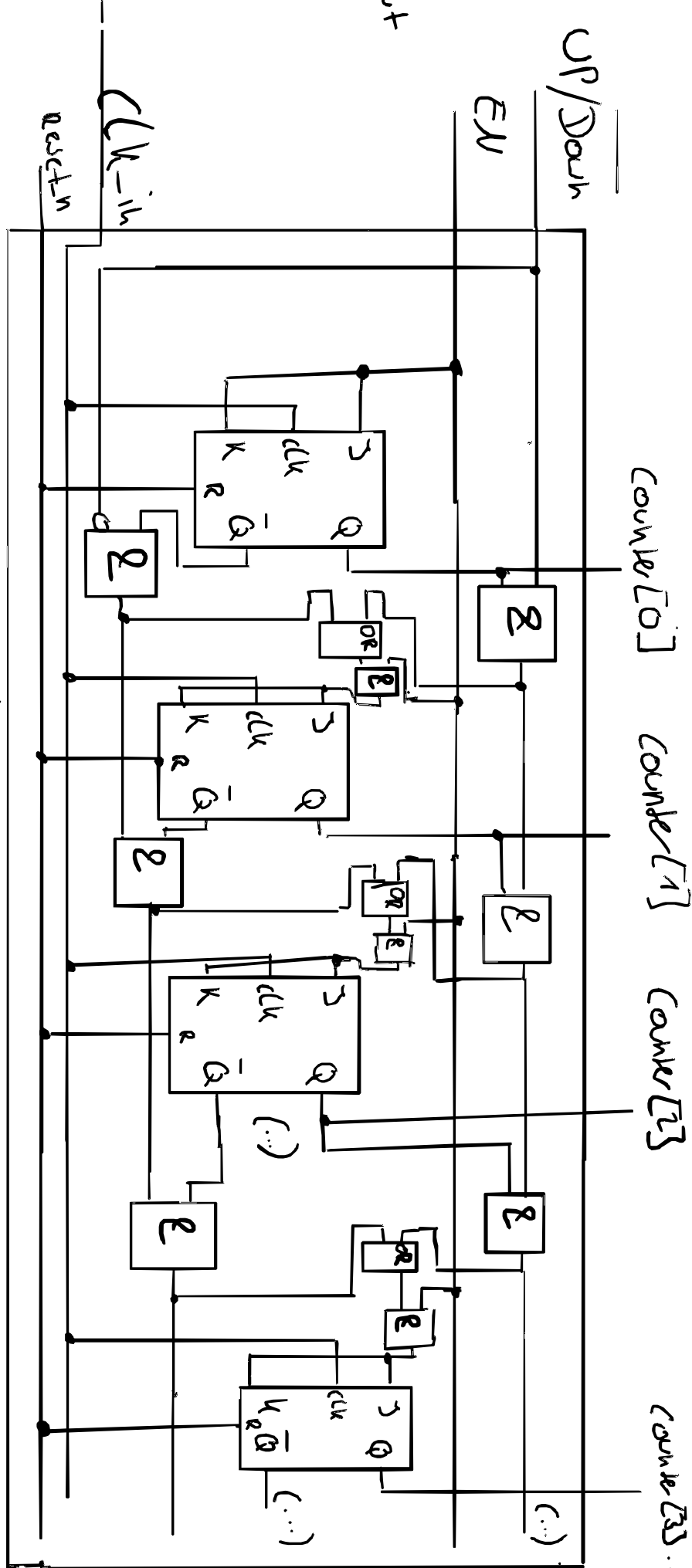

(Simple) Clock Frequency Divider

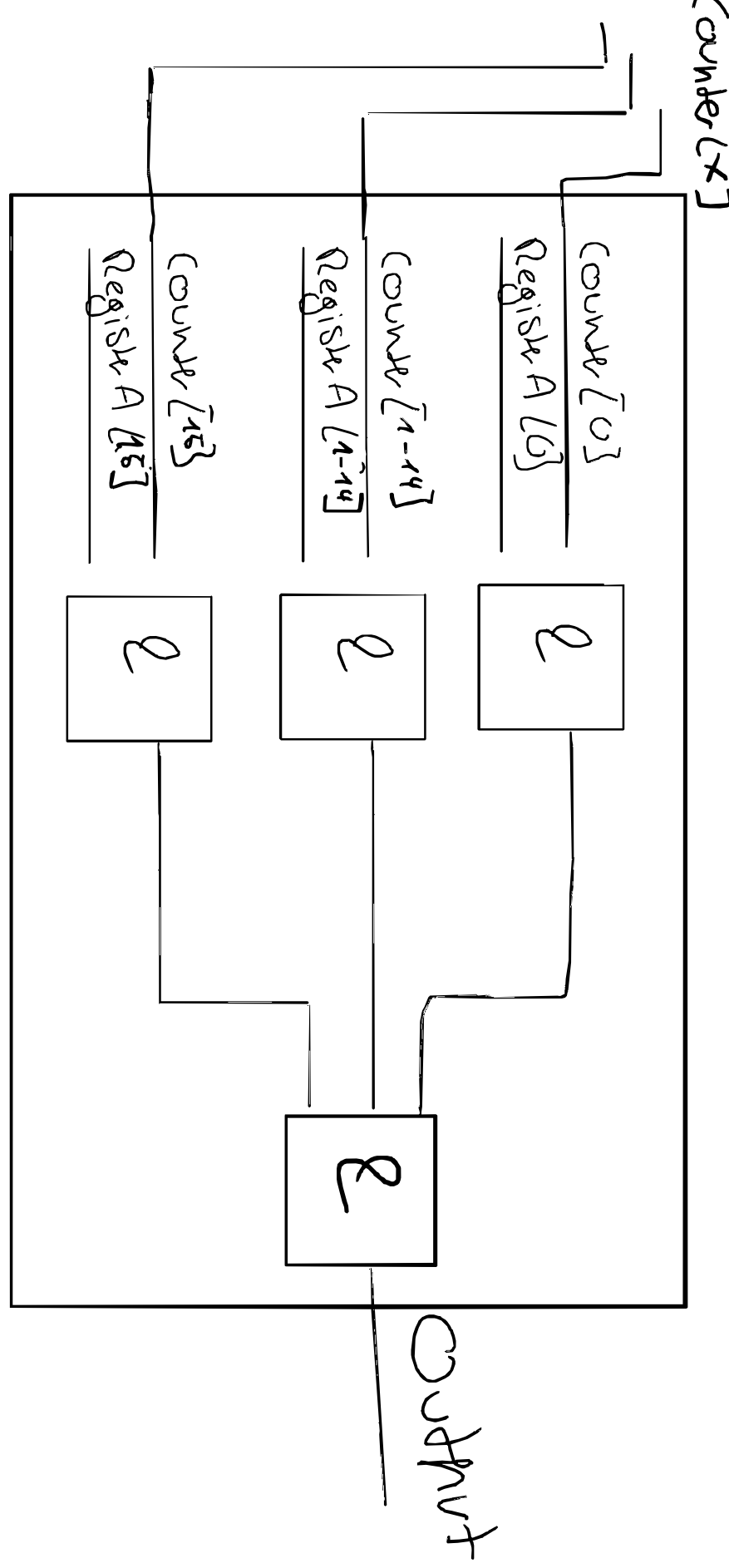


Counter



Output Compare Unit

JK-Flip-Flop:

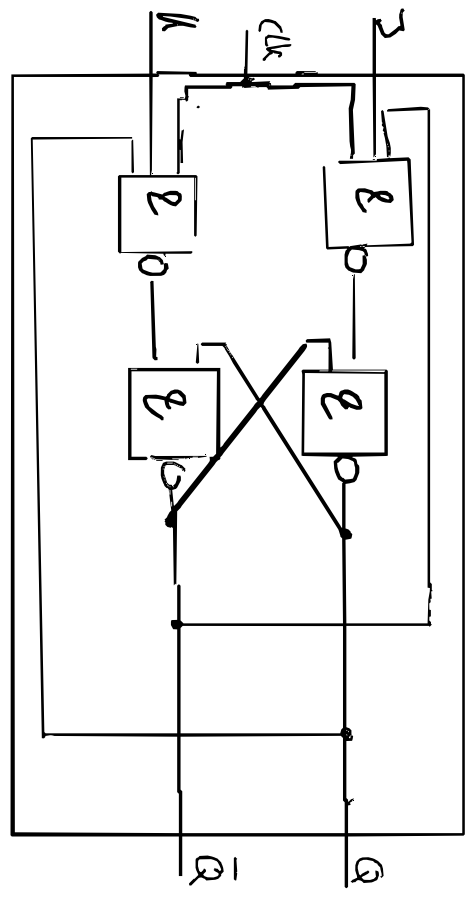

clk	J	K	Q	$\bar{Q}$
1	0	0	Q	$\bar{Q}$
1	0	1	0	1
1	1	0	1	0
1	1	1	Toggle	Toggle
0	X	X	-	-

→ We can use this for our counter